


Assignment9

Abhay Suresh

4th January 2021

1 Assigned Question

The value of F is

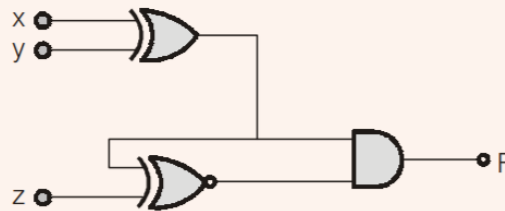

(a) $X \bar{Y} Z + \bar{X} Y Z$

(b) $\bar{X} \bar{Y} Z + \bar{X} Y \bar{Z}$


(c) $\bar{X} \bar{Y} \bar{Z} + X Y Z$

(d) $X \bar{Y} \bar{Z} + \bar{X} Y \bar{Z}$

2 Solution - Forming the Boolean Equation

From the Given logic gate we can identify three different logic gates XOR, XNOR and AND gate using X,Y,Z as variables and F as the output.

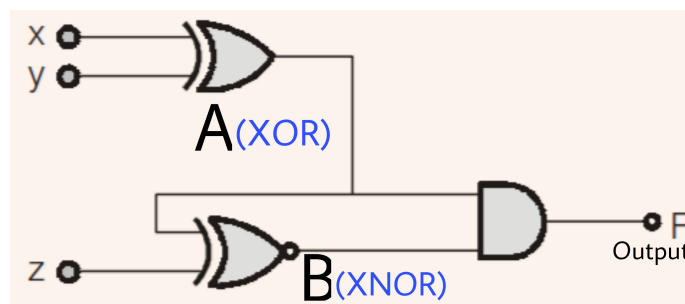Let us represent these Logic gates as A and B, as shown in the following figure.



The Output from A (XOR), where X and Y are the inputs, can be written as

$$A = (\bar{X}Y + X\bar{Y})$$

Similarly the output from B (XNOR), where A and Z are the inputs can be written as

$$B = (AZ + \bar{A}\bar{Z})$$

Now A and B are the inputs for the required Output F which is

$$F = (AB)$$

From the previously obtained Boolean equations for A and B,

$$F = [(\bar{X}Y + X\bar{Y})(\bar{X}Y + X\bar{Y})Z + (\bar{X}Y + X\bar{Y})\bar{Z}]$$

3 Truth Values of the Boolean Equation

The obtained Boolean equation can be simplified further using a K-Map using the Truth Table of the Boolean Equation.

The Truth table values of the boolean equation has been found using a C code for the boolean equation which is mentioned in Section 5

Input			XOR Output	XNOR Output	Final Output
X	Y	Z	A	B	F = A.B
0	0	0	0	1	0
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	1	0	0
0	1	1	1	1	1
1	0	1	1	1	1
1	1	0	0	1	0
1	1	1	0	0	0

4 Simplified Equation using K-Map

From the Truth table obtained for the Logic Gates we can Simplify the respective Boolean Equation using K-Map, using the variables X, Y, Z.

		YZ			
		00	01	11	10
X	0	0	0	1	0
	1	0	1	0	0

The above obtained K-Map gives two terms in SOP as
 $F = (\bar{X}YZ + X\bar{Y}Z)$ which is option (a).

5 C Code used to obtain the Truth Table in Section 3 and Verify the Final Boolean Equation

```

1 //This C program is used to verify the obtained boolean eq(
  unsimplified) of the logic gate from Assignment 9 and to derive
  its Truth Values(EC2014,14)
2
3 #include <stdio.h>
4
5 //The main function
6 int main(void)
7 {
8   unsigned char X=0x01,Y=0x01,Z=0x00;//inputs in hex
9   unsigned char one = 0x01;//used for displaying the output in bit
10  unsigned char A,B,F;//outputs
11
12      A = ((~X)&Y)|((~Y)&X);
13      //XOR GATE
14
15      B = (A&Z)|((~A)&(~Z));
16      //XNOR GATE
17
18      F = A&B;
19      //Final output F (AND GATE)
20
21  printf("The following is the Input for the Logic gate for the
    Assignment 9,represented using X,Y,Z\n\n");
22  printf("X = %x Y = %x Z = %x",one&X,one&Y,one&Z);//Intput XYZ
23  printf(" \n");
24  printf("\n The output of the logic gate, ");
25  printf("F = %x\n",one&F);//Output F
26  printf(" \n");
27  printf("Similarly,rest of the values of input XYZ has been pre
    verified using this C program");
28  return 0;
29 }

```